

# Design of Linear Voltage Regulators

Dipl. Ing. Ricardo Erckert

Ingenieurbüro Erckert  
Harthausenstraße 36 b  
83043 Bad Aibling

Tel.: 08061 392208  
Mobil: 0179 5308708  
email: [re@erckert-ibe.de](mailto:re@erckert-ibe.de)



Ingenieurbüro Erckert  
Ricardo Erckert

16.07.2003


## How do tolerances of voltage regulator and reset generator comply with the application?

- Your application needs a certain minimum supply voltage.
- The lowest possible reset threshold must be above this application limitation.
- The reset generator has a hysteresis. The worst case upper threshold must be below the lowest possible regulator output voltage.
- The regulator accuracy depends on bandgap tolerance, trimming, load rejection, supply rejection and temperature coefficients
- You need margin for dynamic effects



The following presentation gives you an idea how to set up a reasonable voltage regulator specification


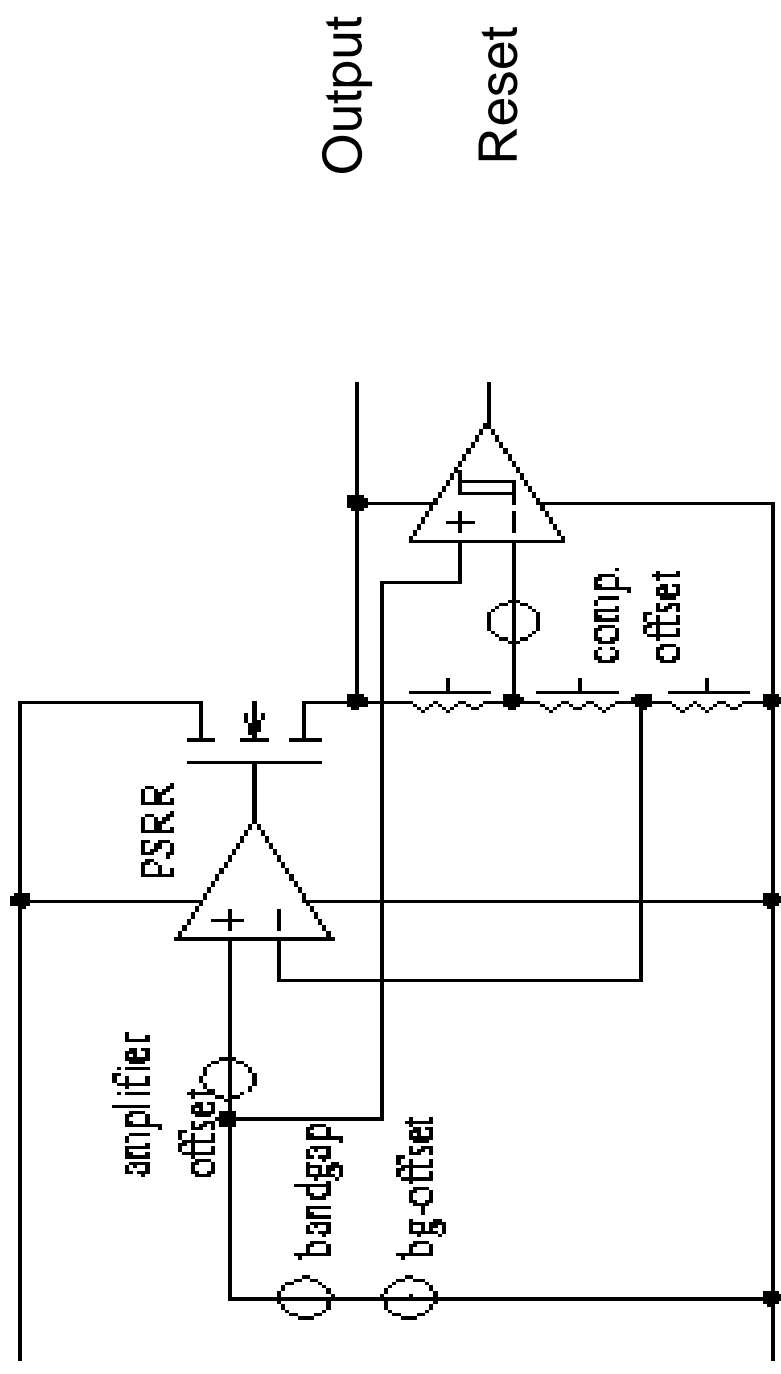
# A typical Voltage Regulator Topology including some Error Sources


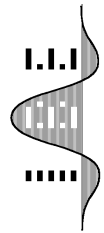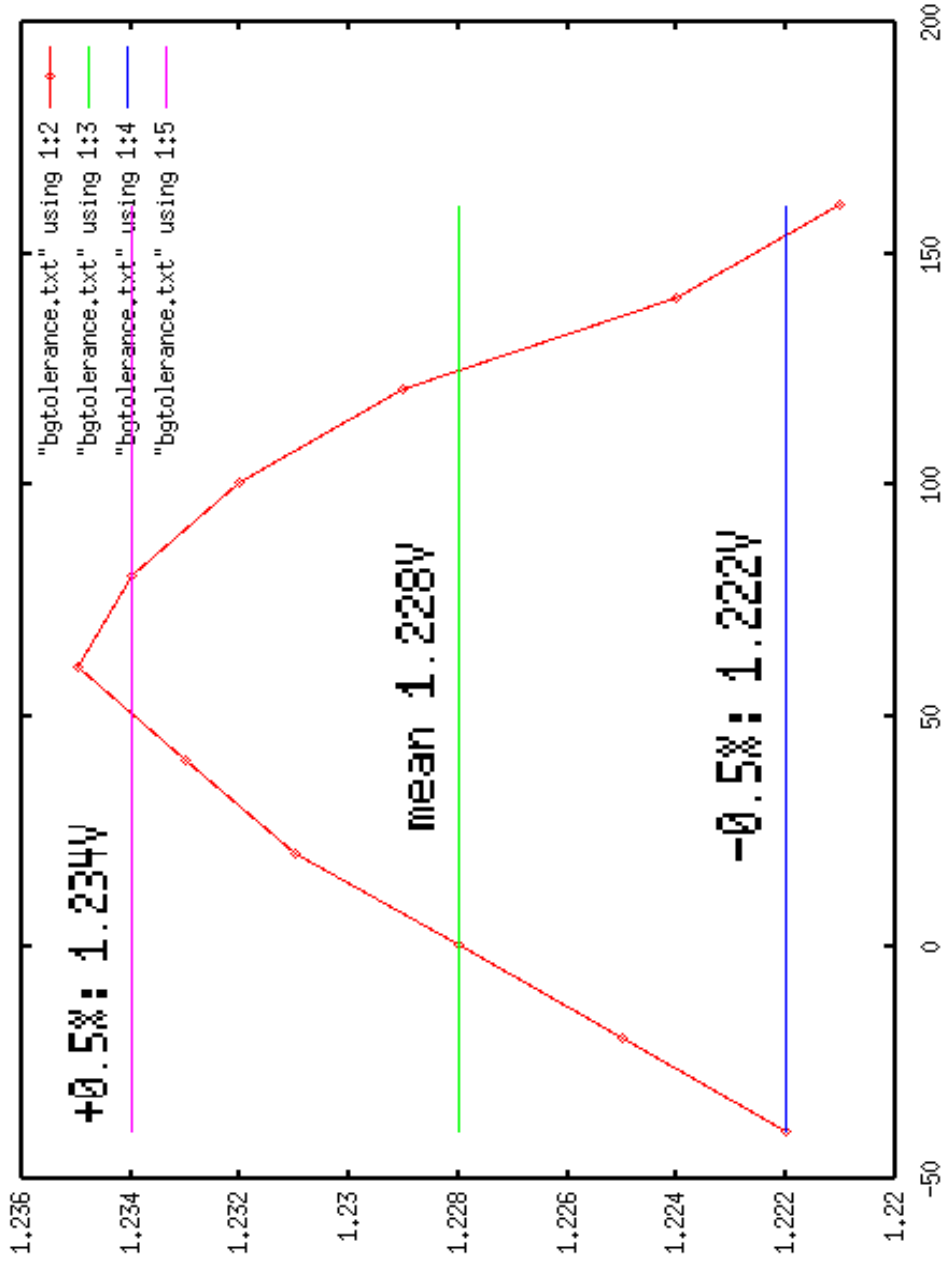
# A Good Bandgap's Temperature Behaviour:



## Load Rejection:

Changing load currents require different output voltages of the regulator driving the power transistor gate. As a rule of thumb the static load rejection calculates as :

$$\Delta V / \Delta I = 1 / (g_m \cdot \text{gain})$$



Or: If your load current changes by  $\Delta I$  your output voltage changes by  $\Delta V$

$$\Delta V = \Delta I / (g_m \cdot \text{gain})$$

(Example:  $g_m=0.025\text{A/V}$ ,  $\Delta I=0.1\text{A}$ ,  $\text{gain}=100 \rightarrow \Delta V=40\text{mV}$ )





# A Practical Example of Load Rejection

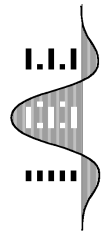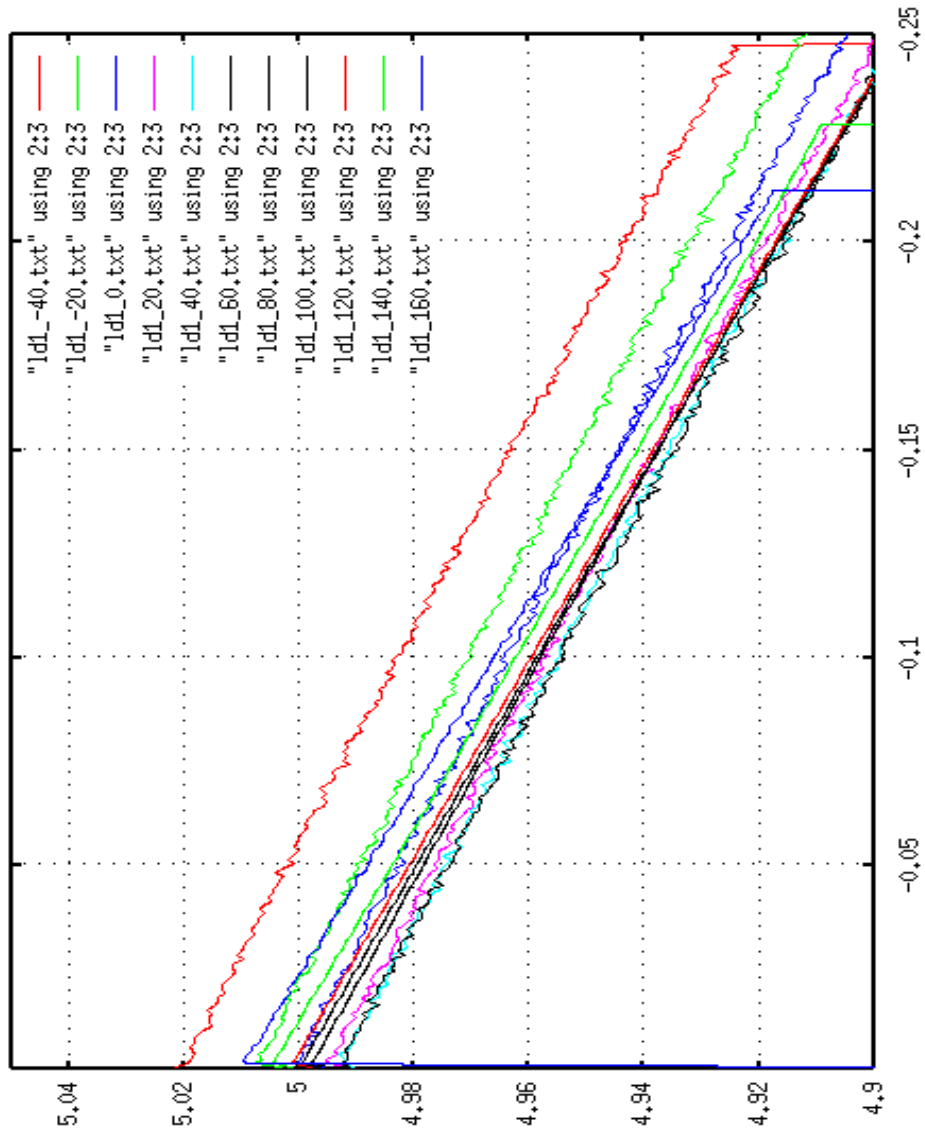

Ingenieurbüro Erckert  
Ricardo Erckert

16.07.2003
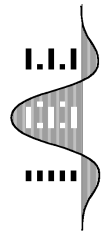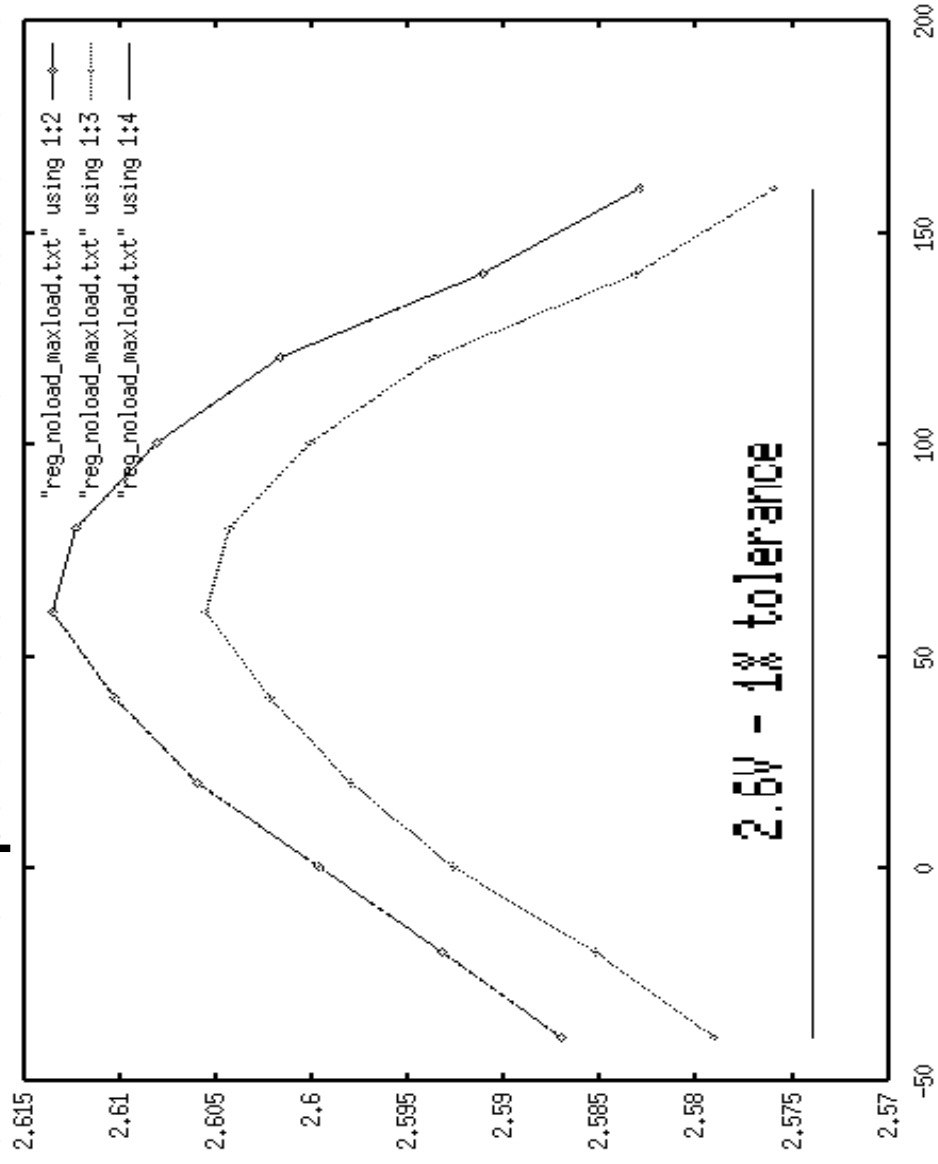
# Regulator w.r.t Temperature at minimum load and maximum load





Ingenieurbüro Erckert  
Ricardo Erckert

16.07.2003

Besides load current supply voltage influences the output voltage of a regulator. Supply rejection depends on early voltages of the transistors used, the amplifier gain and whether cascodes are used. Good regulators have DC supply rejections of 60dB to 70dB. Assuming a 20V supply voltage change 20mV output voltage change must be expected.

## Supply Rejection

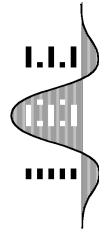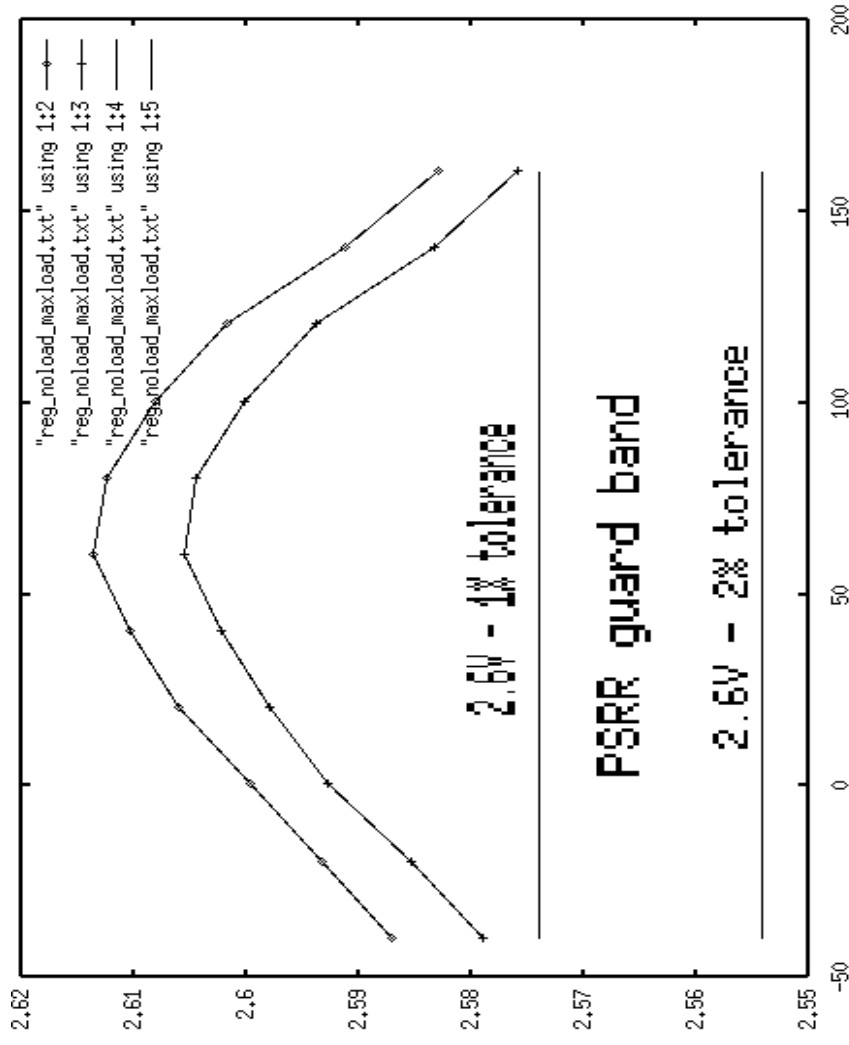



## Bandgap Tolerances

Bandgap accuracy analog process (untrimmed):  $\pm 4\%$

Bandgap accuracy digital process (untrimmed):  $\pm 6\%$

Theoretically you can trim to almost any accuracy you like. But packaging with its mechanical stress will change your parameters again. Packaging can change your bandgap again by 0.2%. So a least significant trim bit below 0.1% doesn't make sense anymore.

Trimmed bandgap after packaging:  $\pm 0.3\%$

### **Conclusion:**

***eventually the regulator tolerance is  $\pm 1.3\%$  to  $\pm 2.3\%$ .  
you can make the typical output voltage without load slightly higher to  
beautify tolerance to obtain  $\pm 2\%$***



Ingenieurbüro Erckert  
Ricardo Erckert

16.07.2003


## Dynamic Behaviour

The speed of a regulator amplifier is limited. At sudden load changes the blocking capacitor must supply the load.

Approximate dynamic change of the output voltage:

$$\Delta V = \Delta I * t_{\text{delay}} / C$$

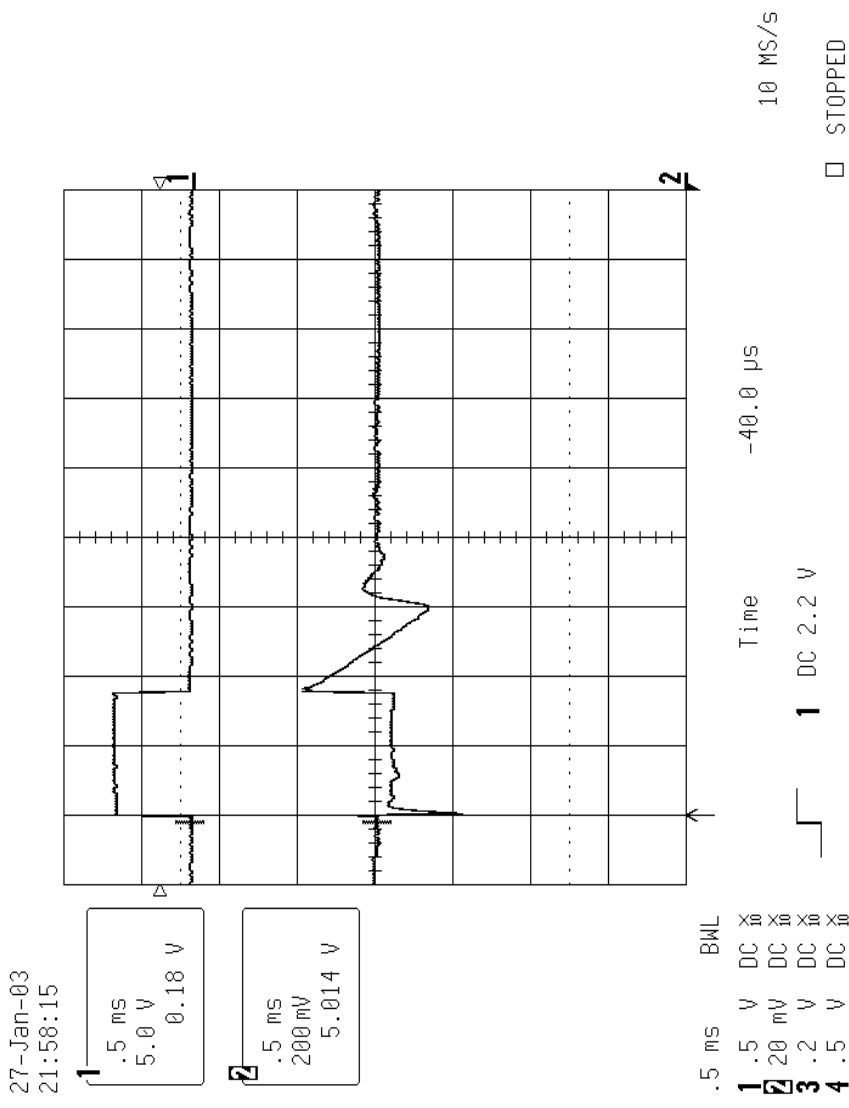(Example:  $\Delta I = 0.1 \text{ A}$ ,  $t_{\text{delay}} = 10 \mu\text{s}$ ,  
 $C = 10 \mu\text{F} \rightarrow \Delta V = 0.1 \text{ V}$ )



## Reset generator

Reset MUST release below the lowest possible output voltage. This is the upper one of the two hysteresis levels.

Resistors can be matched to  $\pm 0.2\%$   $\rightarrow$  add 0.2% margin

Comparator offset can be in the range of 20mV  $\rightarrow$  add 1% margin.

Margin for abrupt load changes and ringing 2%

$\Rightarrow$  Typical reset release threshold must be below 94.8% of the nominal output voltage (2.46V)

Reset hysteresis should be in the range of 50mV. So typical reset trip point is 92.5% (2.405V) of the nominal output voltage. In case tolerance go the other way worst case trip point is as low as 91.3% of the nominal output voltage (2.37V)



## What If You Need Higher Accuracy?

1. Operate the regulator at constant load current. This typically brings a  $\pm 2\%$  device down to  $\pm 1.5\%$  because there is no more error contribution of the load rejection.
2. Supply your regulator from a prestabilized voltage. Together with item 1 you come down to typically  $\pm 1\%$
3. Do You really need the full temperature range? Restricting your application to a smaller temperature swing is helpful.
4. Ceramic packages usually induce less mechanical stress and will in most cases improve accuracy by 0.1% to 0.3%.

